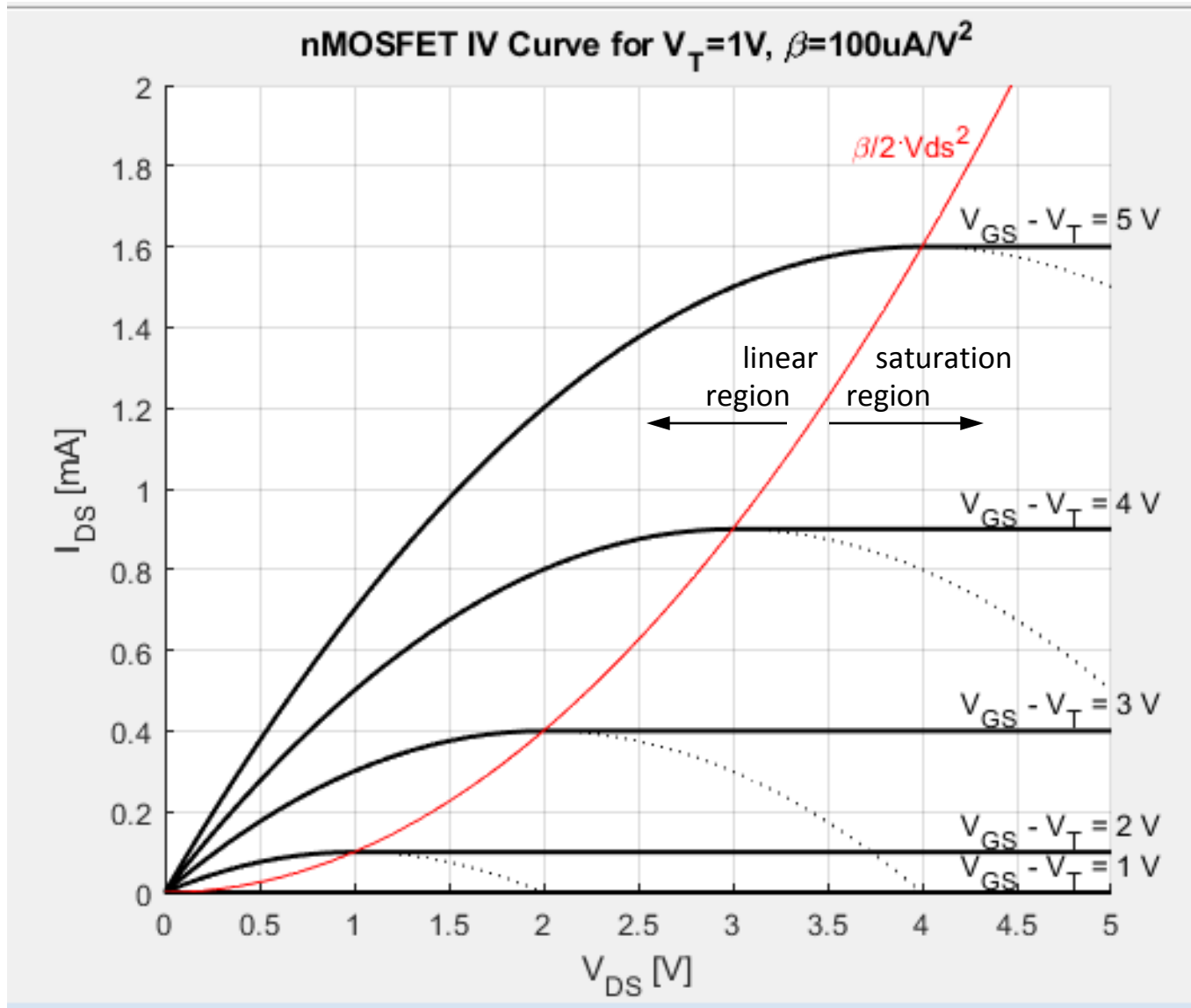


MOSFETs


- nMOS
 - Threshold Voltage:
 - $V_T = 1.0\text{V}$ (for example)
 - Transconductance Parameter:
 - $\beta = 100\mu\text{A}/\text{V}^2\text{V}$ (depends on process and geometry)
- OFF State $V_{GS} \leq V_T$
 - $I_{DS} = 0 [\text{A}]$
- ON State if $V_{GS} > V_T$
 - “Linear” Region if $V_{DS} < V_{GS} - V_T$
 - $I_{DS} = \beta \cdot [(V_{GS} - V_T) - V_{DS}/2] \cdot V_{DS}$
 - Saturation Region if $V_{DS} \geq V_{GS} - V_T$
 - $I_{DS} = \beta/2 \cdot (V_{GS} - V_T)^2$

nMOSFET IV Characteristic



nMOS Transistor IV Characteristic

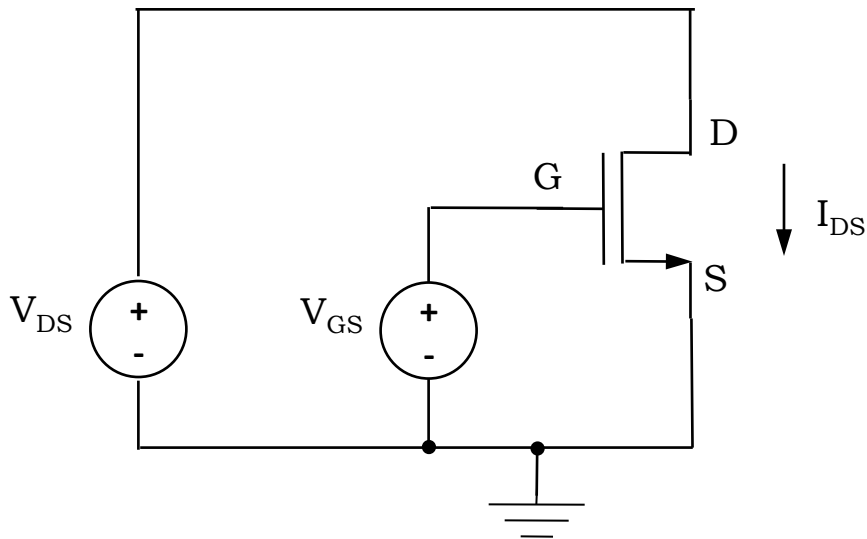
- nMOS
 - as a 3 terminal device
 - G – “gate”
 - S – “source”
 - D – “drain”
 - charge carriers are electrons
 - (negatively charged) electrons flow from source to the drain
 - I_{DS} is drain to source current
 - conventional current



side note:

- In *pMOS* the charge carriers are holes
 - effectively a positive charge
- When nMOS and pMOS are used together it's known as CMOS which stands for Complementary MOS

nMOS Inverter

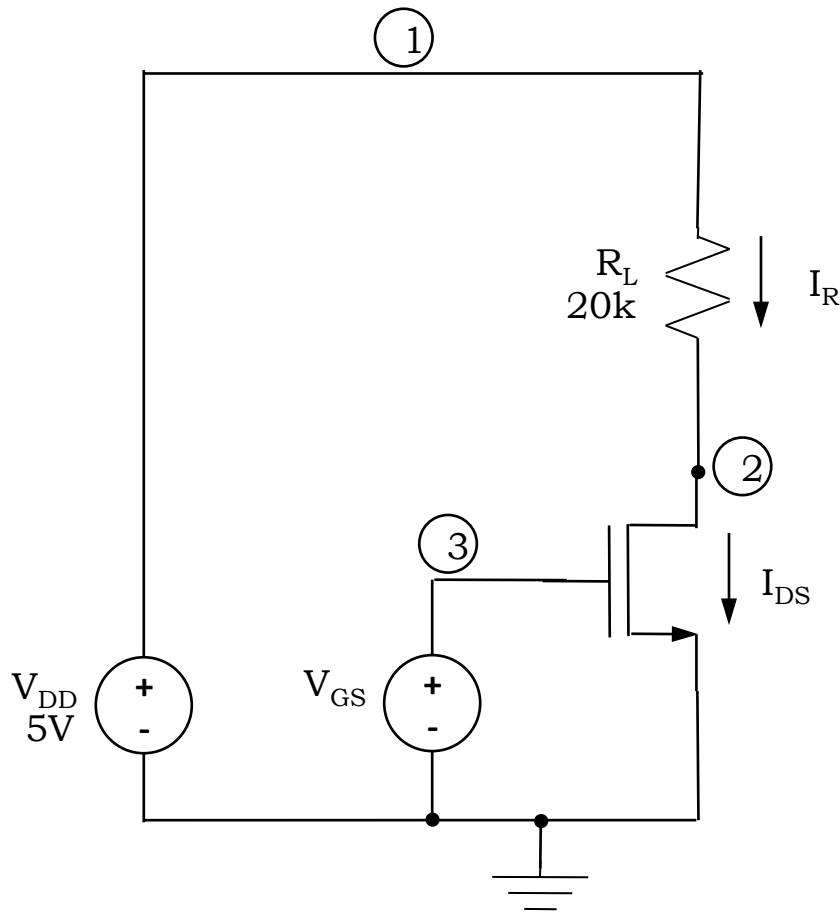

Case 1: $V_{GS} = 5V$

Is transistor in linear or saturation?


Let's find I_{DS} if transistor is in saturation:

$$\begin{aligned} I_{DS} &= \beta/2 \cdot (V_{GS} - V_T)^2 \\ &= 100\mu A/V^2 / 2 \cdot (5V - 1V)^2 \\ &= 1.6mA \end{aligned}$$

But this would mean voltage drop across $V_{RL} = I \cdot R = 1.6mA \cdot 20k\Omega = 32V$! This can't be, because the power supply (V_{DD}) is 5V. The maximum current which could flow through R_L is $I_{Rmax} = V_{DD}/R_L = 5V/20k\Omega = 250\mu A$

[note: $I_R = I_{DS}$]

nMOS Inverter

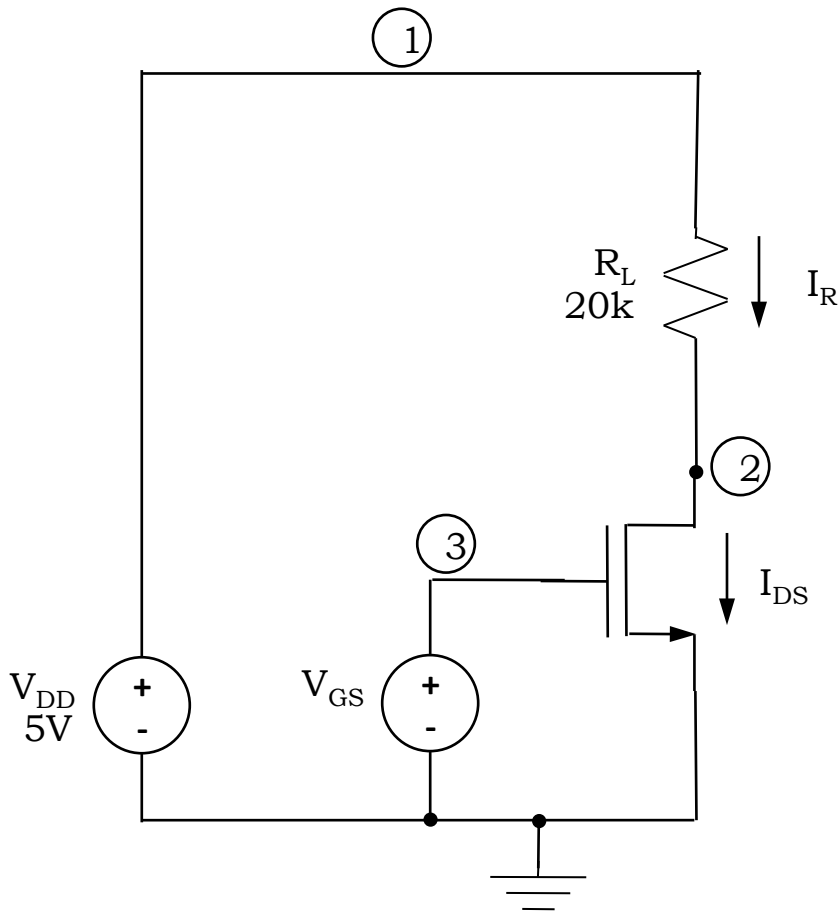


Case 2: $V_{GS} = 0$
from transistor characteristic:
 $I_{DS} = 0$ (and thus $I_R = 0$)
Thus $V_R = 0$ and $V_2 = 5V$

That is, the MOSFET is in the OFF state, so no current flows, and thus no current flowing in the resistor. If a resistor has no current flowing through it, the voltage (drop) across it is zero. Thus voltage at node 2 and voltage at node 1 are equal.

ON Resistance


- Linear Region: $I_{DS} = \beta \cdot [(V_{GS} - V_T) - V_{DS}/2] \cdot V_{DS}$
 - **If** $V_{DS}/2$ is very small compared to $V_{GS} - V_T$, then I_{DS} can be approximated as:
 - $I_{DS} = \beta \cdot (V_{GS} - V_T) \cdot V_{DS}$
- This now looks like Ohm's Law, stated as $R=V/I$
 - So, $R_{ON} = V_{DS} / I_{DS} = 1 / [\beta \cdot (V_{GS} - V_T)]$

nMOSFET IV Characteristic

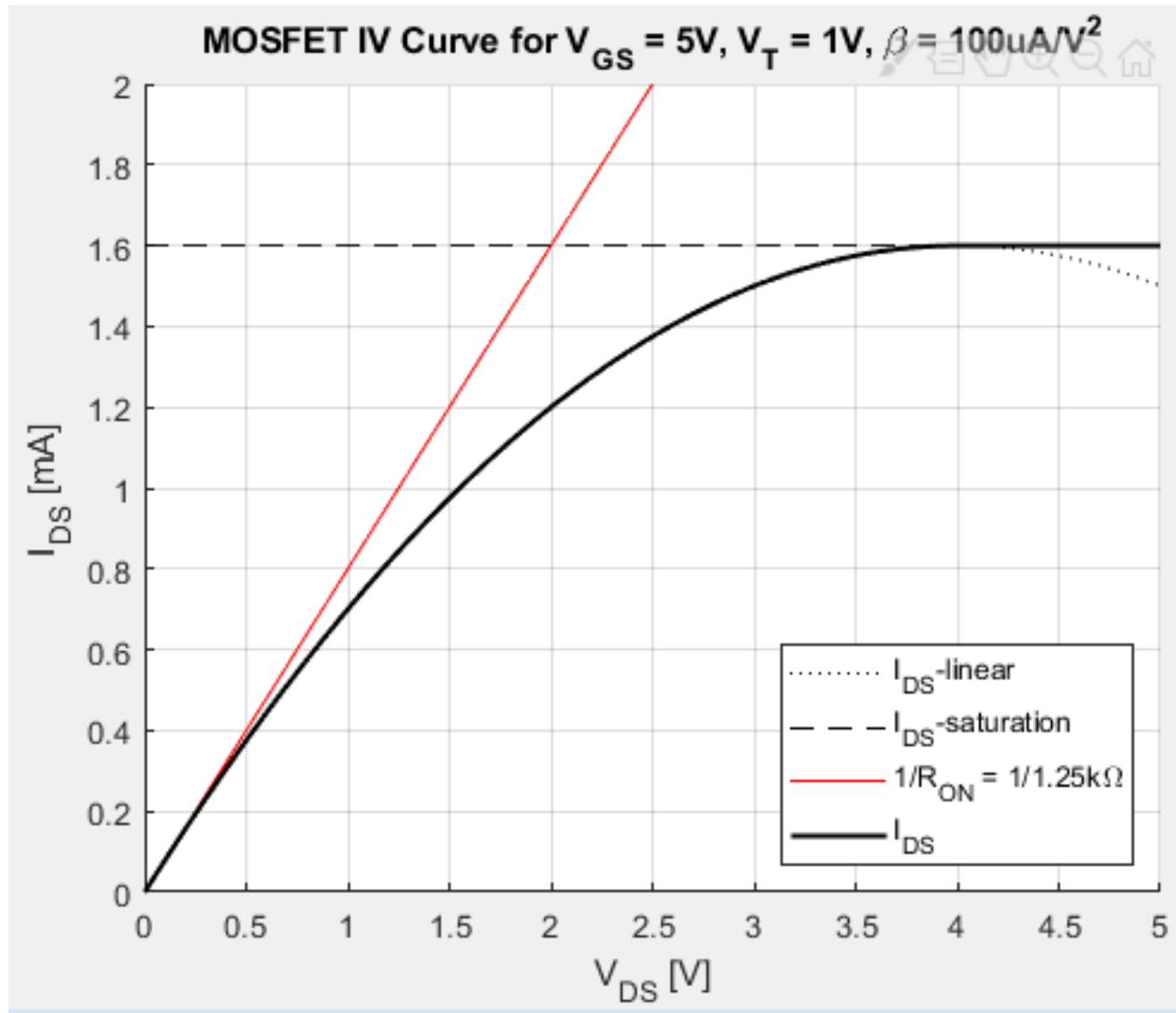

Diodes

Diode IV Characteristic – Forward Bias

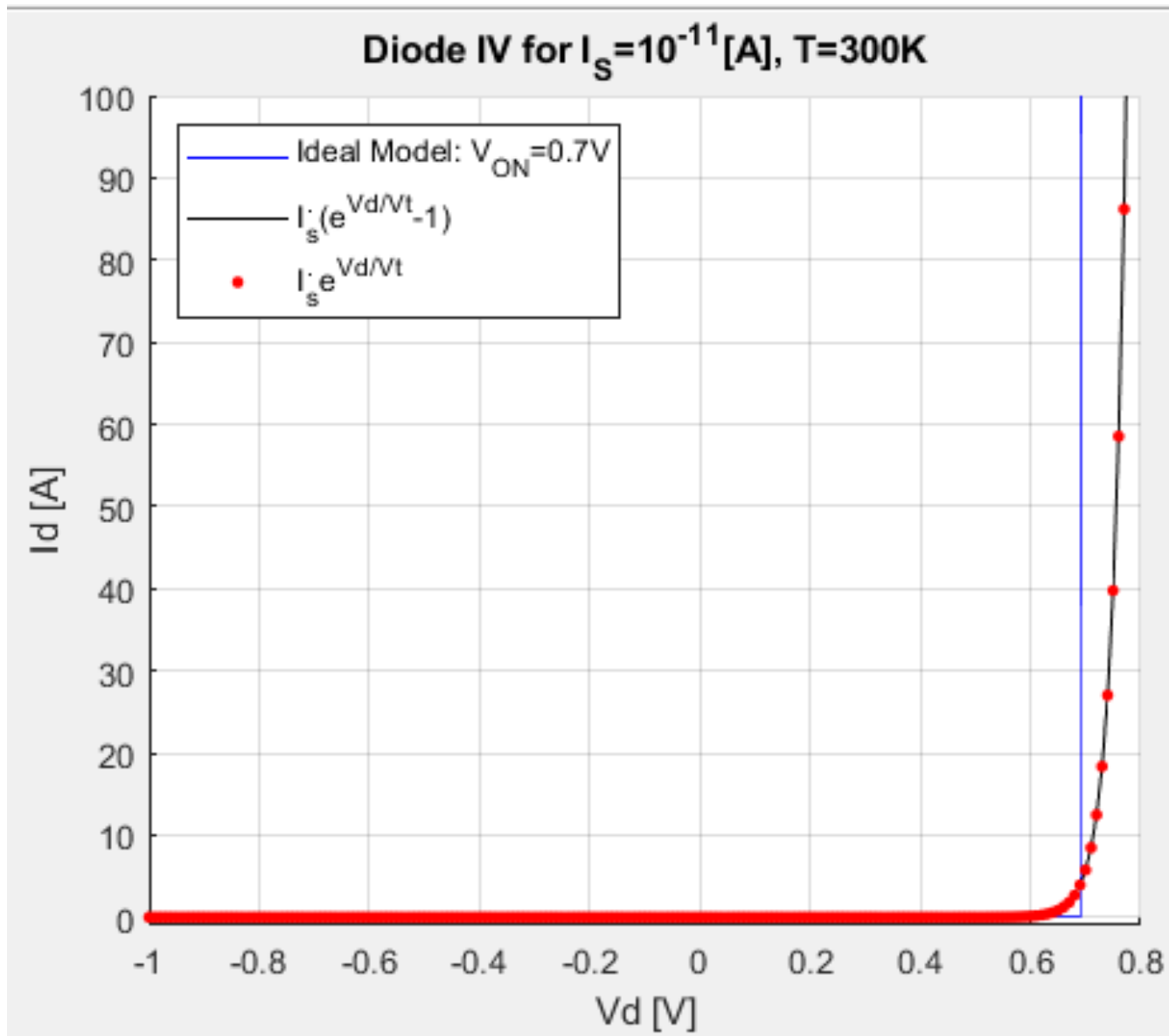

Diode IV Characteristic – Reverse Bias

